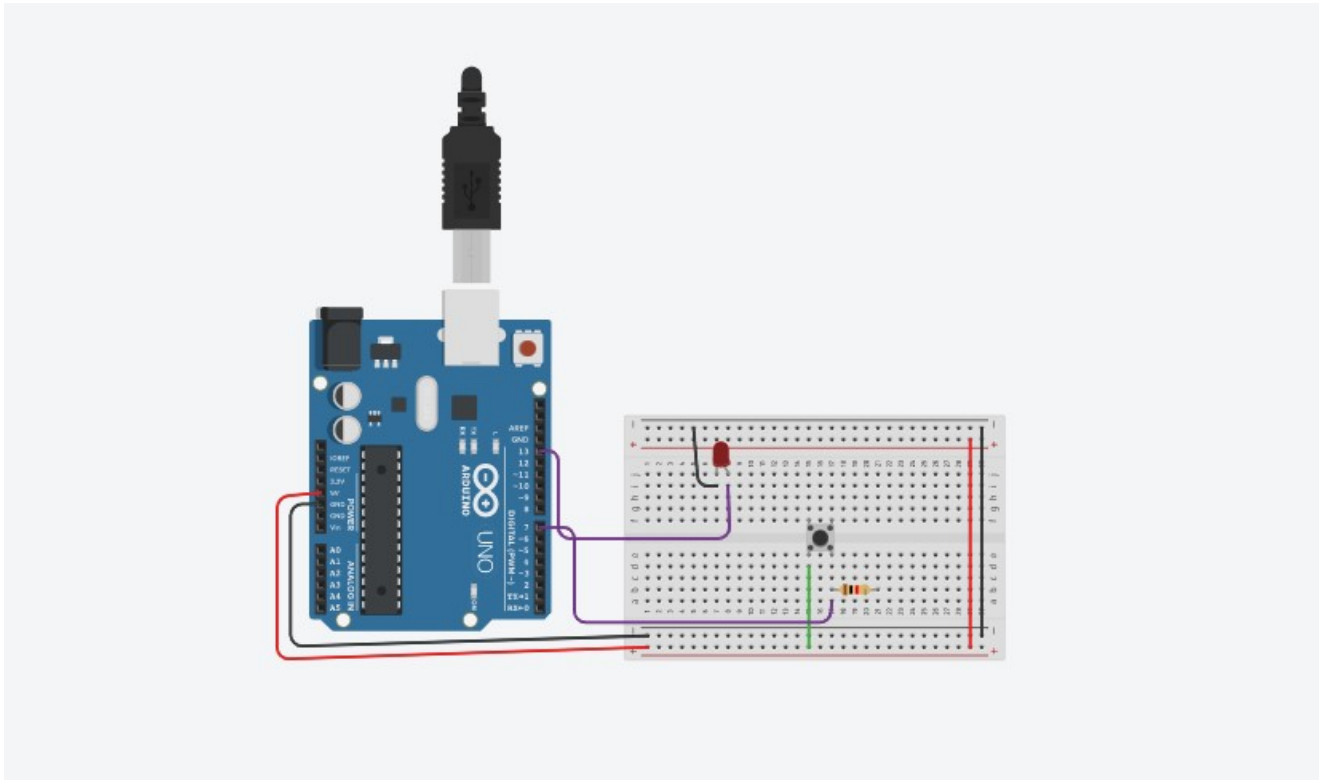


Button controlled LED

Circuit Diagram:



TheoryConcept

Used:

The LED turns on when the button is pushed and turns off when the button is released.

Learning and Observations:

Following observations were recorded during the experiment:

- ❖ *The LED turns on when the input from the button is HIGH and turns off when it is LOW.*
- ❖ *The button needs to be connected to the ground to give LOW input when the button is not pressed.*

Problems and Troubleshooting:

The problem faced while performing the experiment was that the program compiled and uploaded to the board successfully but the LED didn't glow. The problem was troubleshooted by replacing a connecting wire.

- *Making a functional was a bit time taking as it becomes a bit confusing on arranging the wires.*
- *Minor errors showed up in the code during the test run, which was trouble shooted by the correcting the above*

Precautions:

The following precautions need to be considered while performing this experiment:

- The connections of the USB in both the PC and the ARDUINO UNO board should be snug.*
- The USB ports of the PC and the ARDUINO UNO should be in a working condition.*
- The sketch should be logically and syntactically correct and germane to the experiment that needs to be performed.*
- The correct serial port should be selected that is the one through which the ARDUINO UNO has been connected.*
- Look for errors during compilation and upload of the executable to the ARDUINO UNO.*
- Disconnect the digital 1 and 0 pins while uploading the program to the board.*
- Do not open more than one instance of the ARDUINO IDE at a time.*

Learning outcomes:

The various learnings as the outcome of performing the above-mentioned experiment are:

- 1. Use of the digitalRead() function.*
- 2. Connecting a push button to take input and send it to ARDUINO.*
- 3. I have learnt to use Arduino Board and how the code will work whenever the switch is pressed LED emits light.*
- 4. How a circuit is placed on breadboard so that it can work properly.*
- 5. Arduino board has Digital pins and Analog pins.*
- 6. Digital pin provides Input as well as Output, but Analog pin provides only input.*
- 7. The Arduino board has ~ sign in Digital pin side which is also known as Pulse Width Modulation (PWM).*
- 8. These pins help's in getting Analog signals with digital means.*

